

Speed Control of Induction Motor

Agenda

- ▶ Getting Started with MATLAB/SIMULINK
 - Power Electronics Devices
- ▶ Design of Single-Phase Inverter
- ▶ Design of Three-Phase Inverter
- ▶ Proportional + Integral (PI) Control
- ▶ Closed Loop Speed Control Squirrel-Cage Induction Motor
 - Stator Voltage (V) Control
 - Frequency (F) Control
 - V/F Control

Introduction to Power Electronics Device

MATLAB/SIMULINK

▶ Design of Electric Circuit.

▶ Uncontrolled Device

- Diodes

▶ Controlled Device


- Thyristor
- Mosfet
- IGBT



Generate Pulses for AC/DC voltage


Circuit - 1

Measure Voltage and Current across R_L

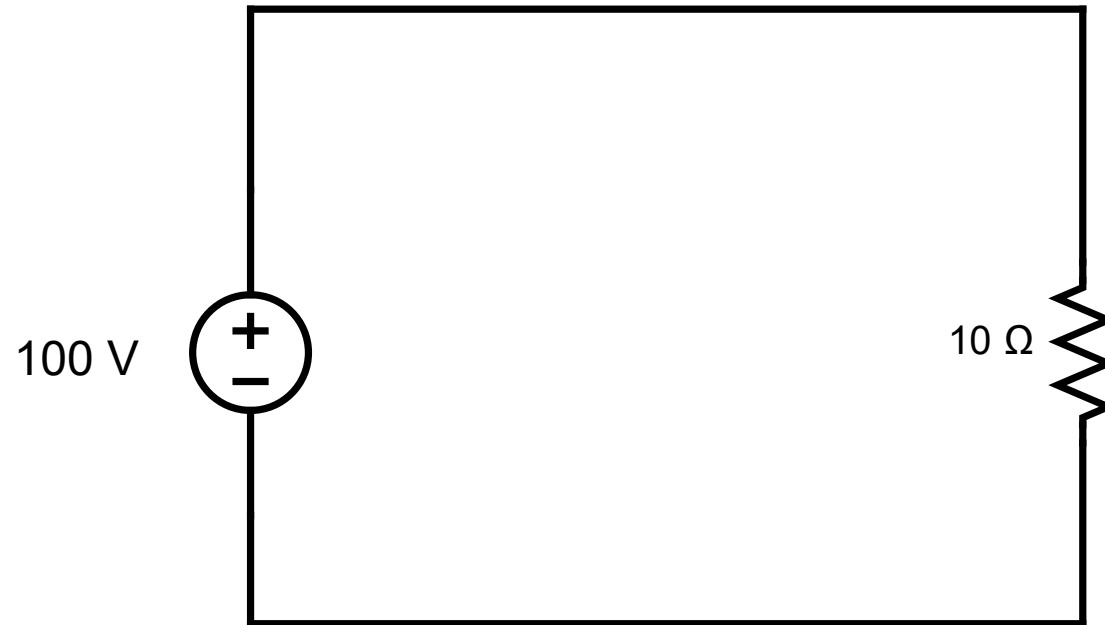

Circuit - 2

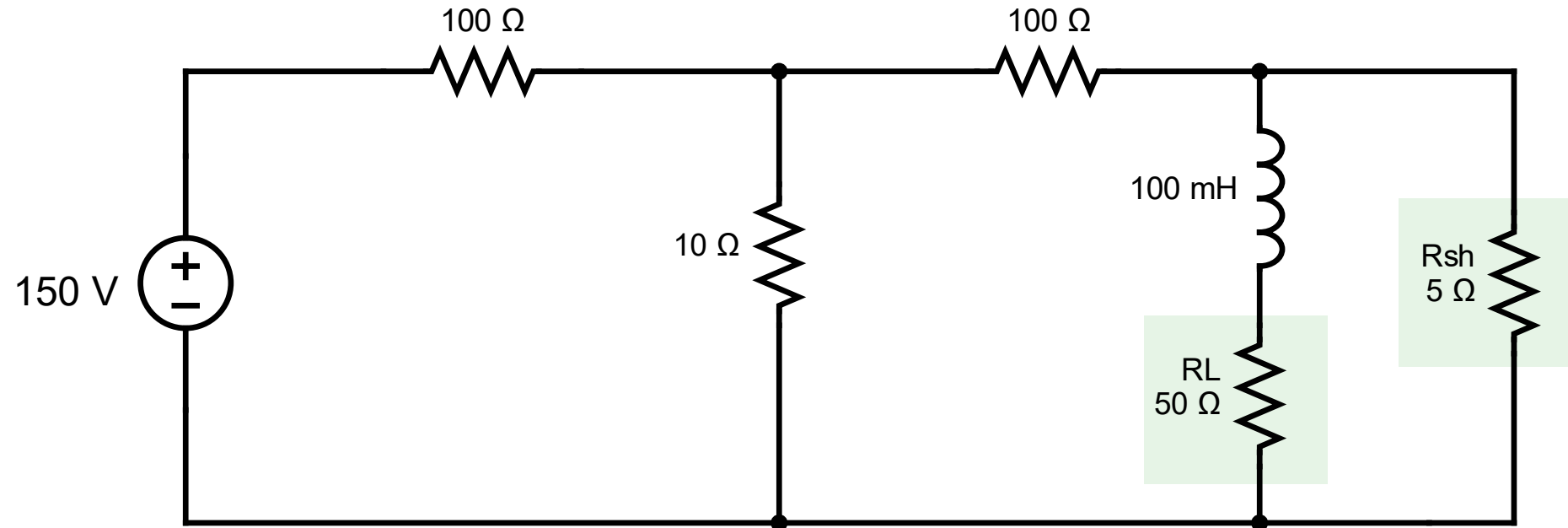Measure Voltage across R_L and current through R_{sh} in SIMULINK



Uncontrolled Devices

Diode Rectifier

Rectifier

A rectifier is a circuit that converts an AC signal into unidirectional signal.

- AC to DC converter


Types of Uncontrolled Rectifier:

- Half Wave Rectifier
- Full Wave Rectifier
- Full Wave Bridge Rectifier

Half Wave Rectifier

CIRCUIT – 1


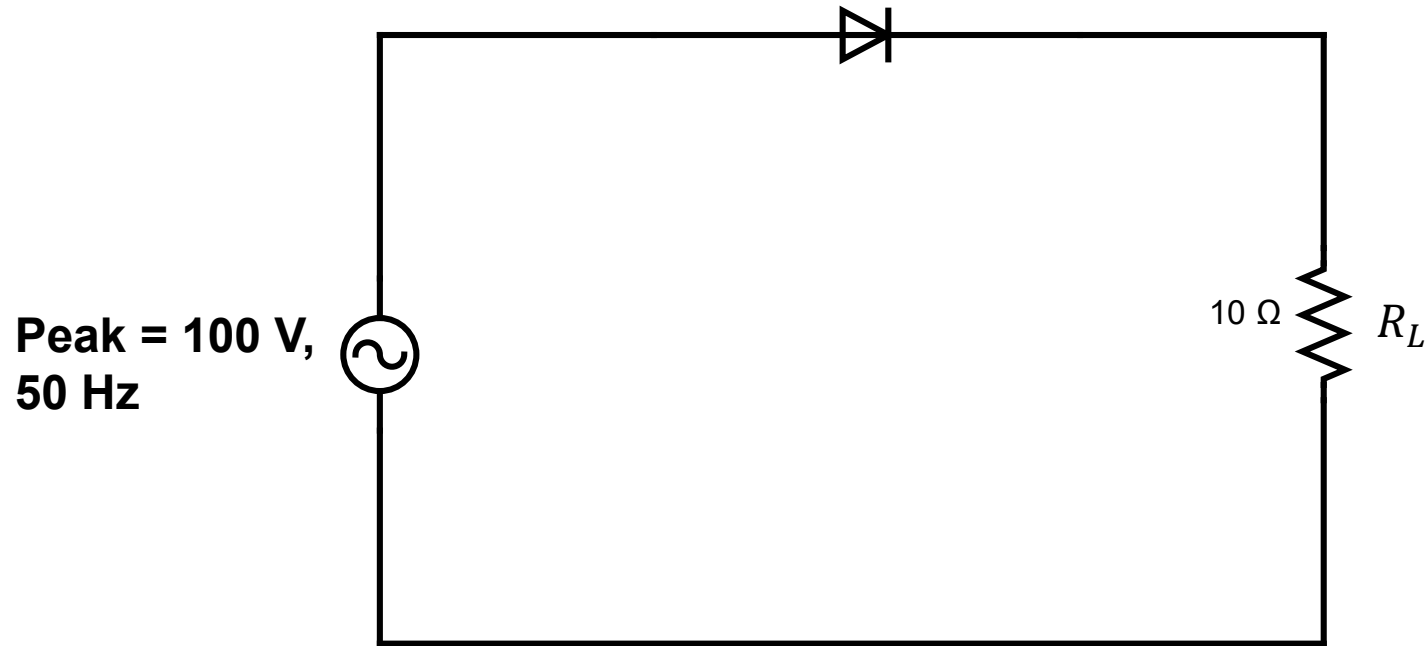
- Visualize voltage and current across R_L



Full Wave Rectifier

CIRCUIT – 2

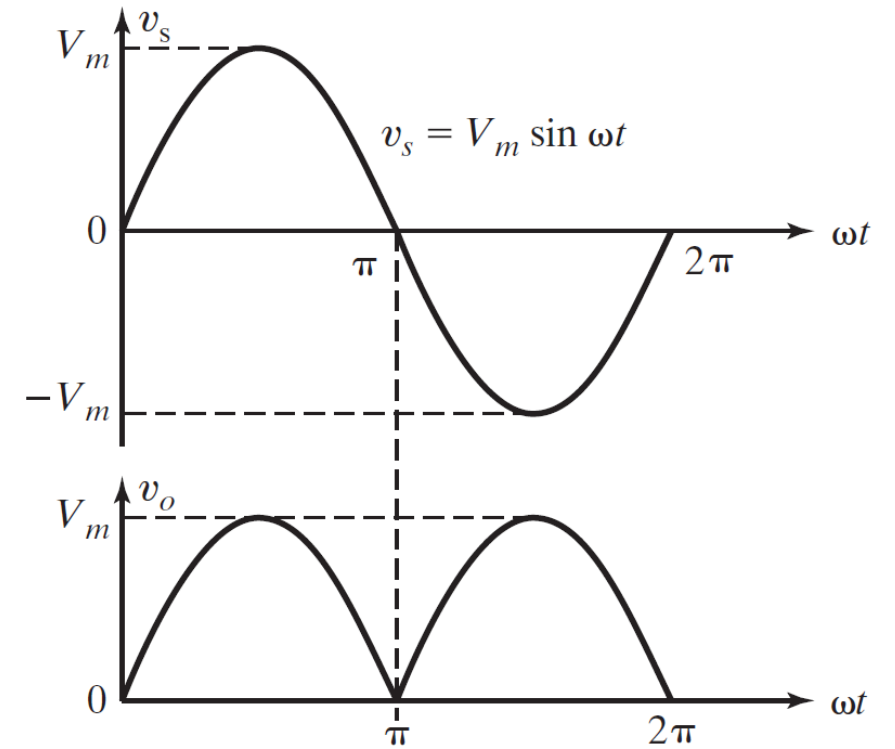
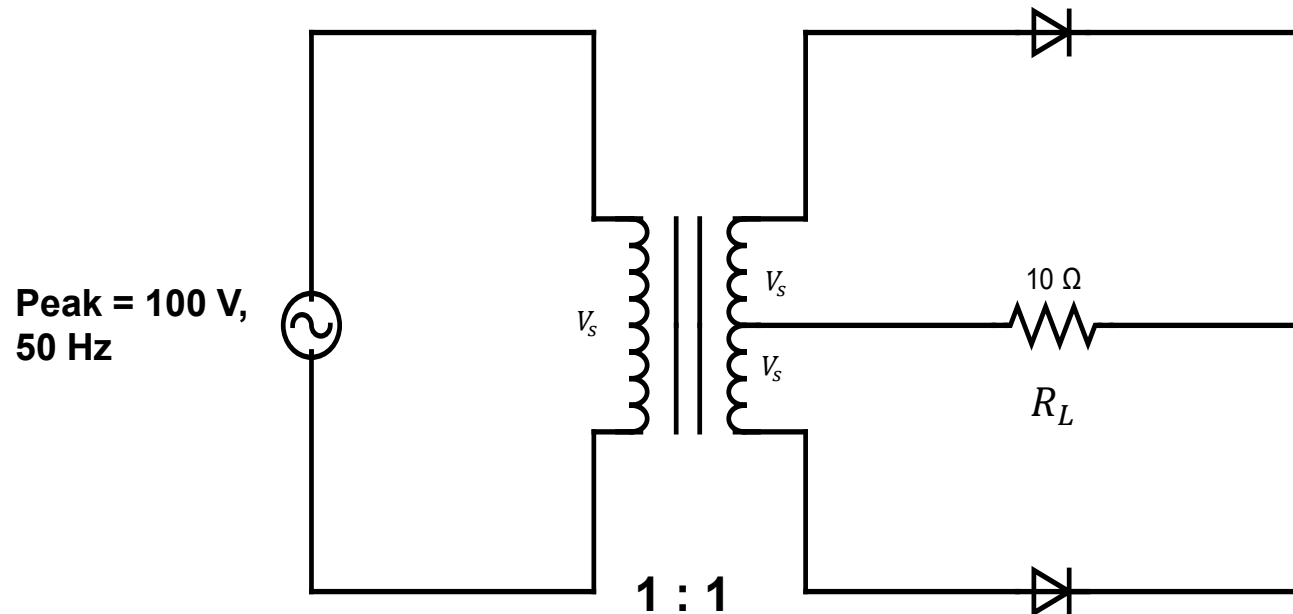
- Visualize voltage and current across R_L



Full Wave Bridge Rectifier

CIRCUIT – 3

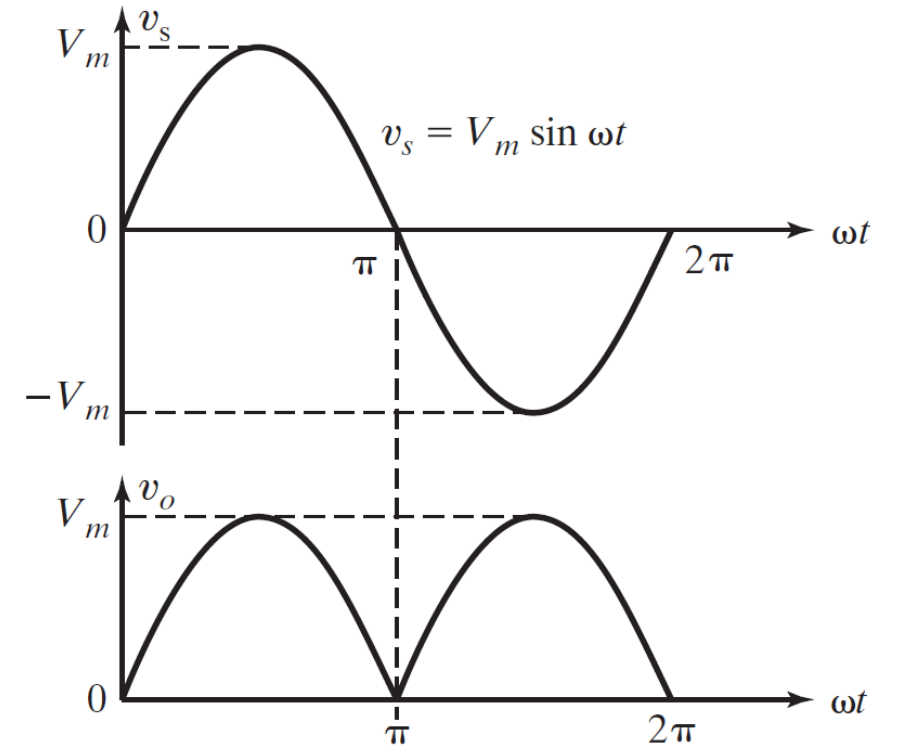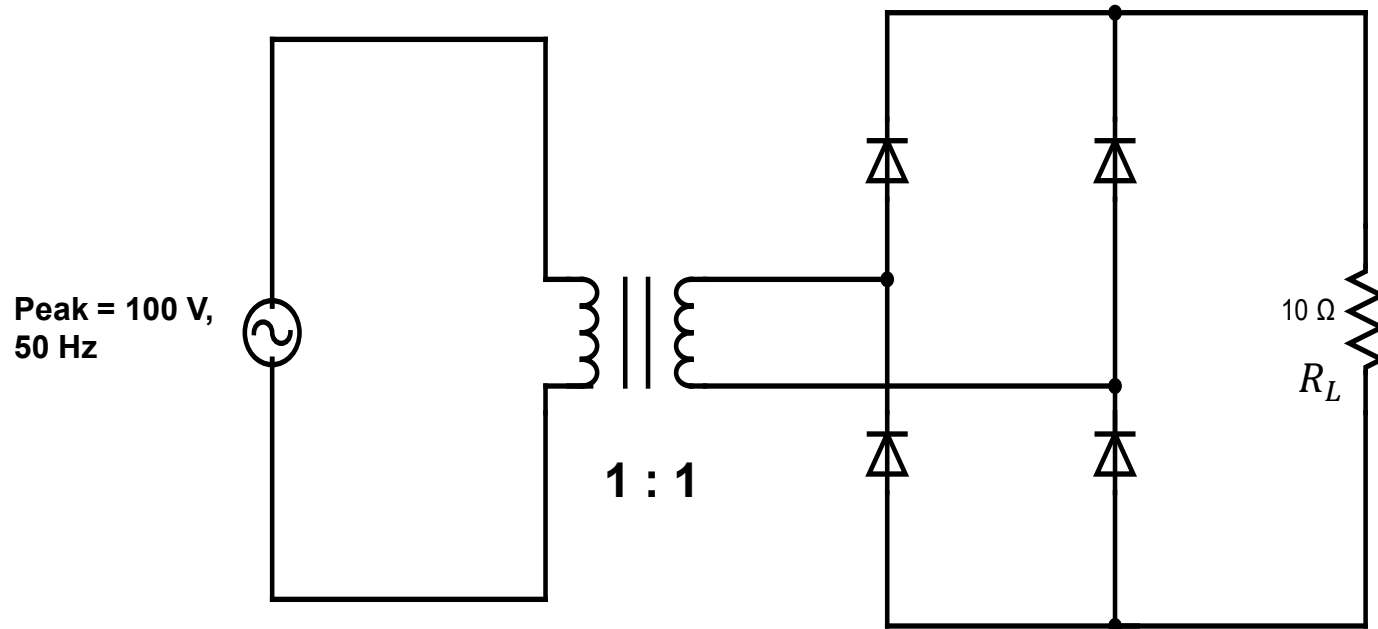- Visualize voltage and current across R_L



Full Wave Bridge Rectifier

CIRCUIT – 4

- Visualize voltage and current across R_L

